
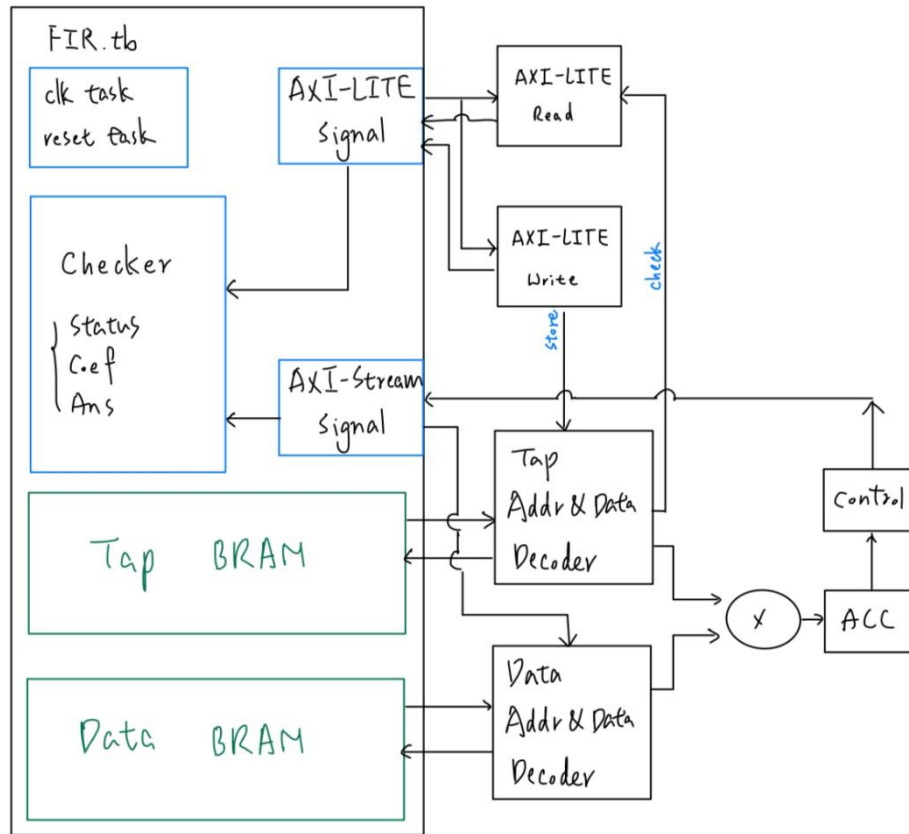


Report

Block diagram:

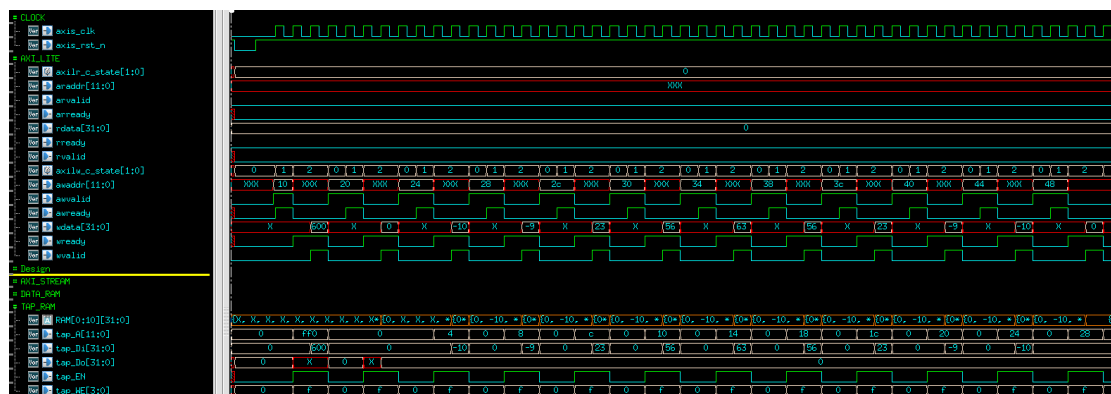


How to receive data-in and tap parameters and place into SRAM?



For AXI-Lite write transaction, I create the FSM to control the signal. When address handshake complete, I can get the correct address and wait for the wdata handshake. Here, I can control the tap WE signal to write mode. Once handshake complete, the

 How to access shiftram and tapRAM to do computation?



```
always@(*) begin
    // default
    save_cnt_n = save_cnt_c;
    get_cnt_n  = get_cnt_c;
    cnt_n      = cnt_c;

    // cnt_n
    if(cnt_c == 12) cnt_n = 0;
    else if(ap_idle == 0 && dbr_c == DBR_IDLE) cnt_n = cnt_c + 1;
    else if(addrTap == 0 && wdata == 1 && wready == 1 && wvalid == 1) cnt_n = 0;

    // save_cnt_n
    if(save_cnt_c == 10 && ss_tready == 1) save_cnt_n = 0;
    else if(ap_idle == 0 && cnt_c == 0 && dbr_c == DBR_IDLE) save_cnt_n = save_cnt_c + 1;
    else if(addrTap == 0 && wdata == 1 && wready == 1 && wvalid == 1) save_cnt_n = 0;

    // get_cnt_n
    if(ss_tready_d1 == 1) get_cnt_n = save_cnt_c;
    else if(get_cnt_c == 10) get_cnt_n = 0;
    else if(ap_idle == 0 && dbr_c == DBR_IDLE) get_cnt_n = get_cnt_c + 1;
end
```

I use three counters to manipulate the SRAM address encoding. The first counter, `cnt_c`, I count from 0 to 12. When count to 0 anytime, the input data from axis-protocol stored into the data SRAM and the `save counter` plus one. At the same time, the third counter, `get counter`, counts starting from the save counter, and the get counter's value is used for the data BRAM address. After the above counters design, I can get the correct data and coefficient at every cycle.


First 13 cycles (2 cycles reserved for read and write)

Data	0	0	0	0	0	0	0	0	0	0	1
Tap	0	-10	-9	23	56	63	56	23	-9	-10	0


Second 13 cycles

Data	0	0	0	0	0	0	0	0	0	1	2
Tap	0	-10	-9	23	56	63	56	23	-9	-10	0

How to control your status signals?

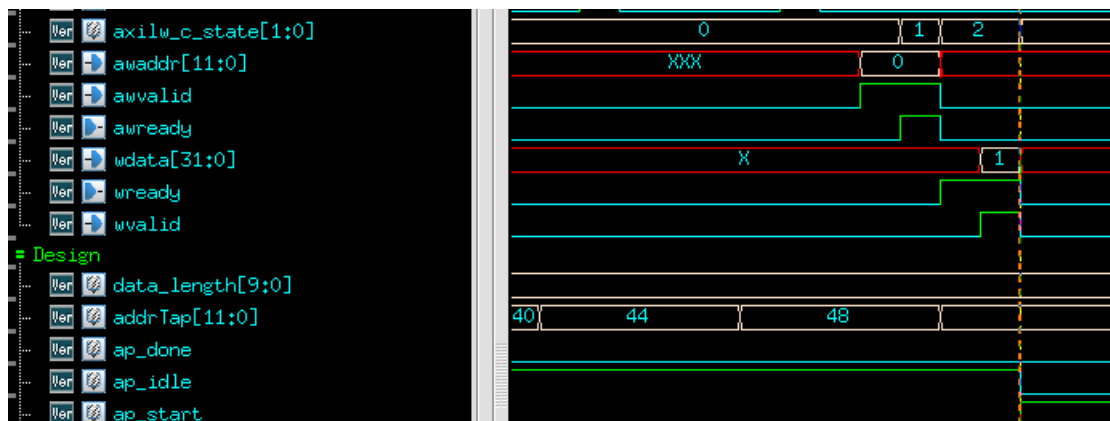

Start signal

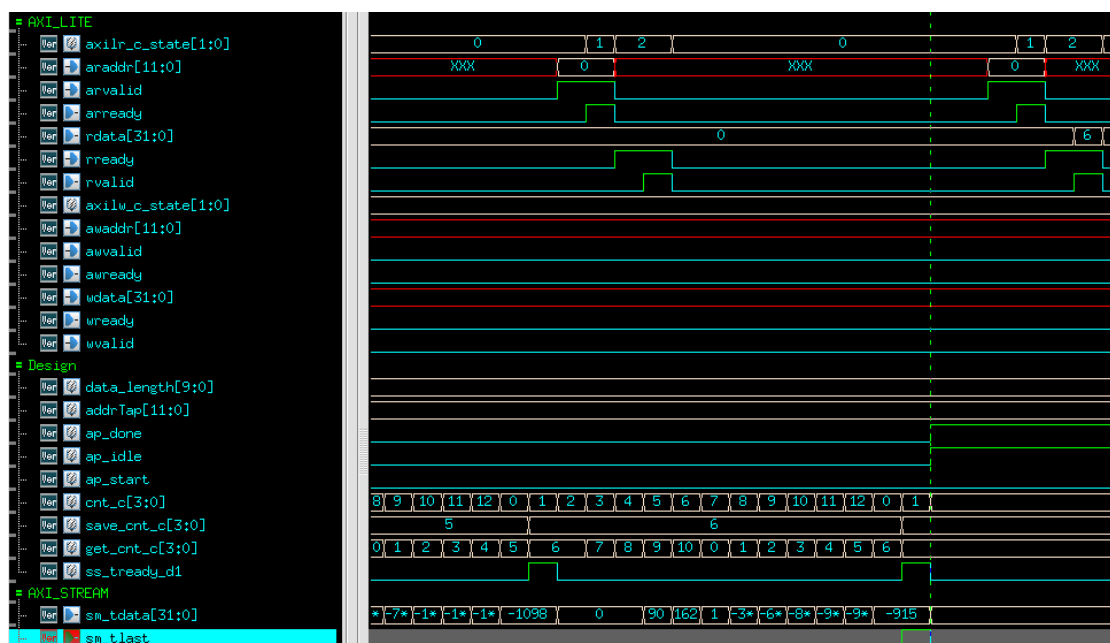

Idle and Done signal

Start signal pulls up when AXI-Lite write transaction writes the 0x00 address and 0 as wdata. Idle and done signals pulls down when the last answer has been transferring out through AXI-Stream transaction. And my status reset method is to wait the fir system get the next start signal then to reset the done and idle signal.

Resource usage: including FF, LUT, BRAM

Site Type	Used	Fixed	Prohibited	Available	Util%
CLB LUTs*	235	0	0	230400	0.10
LUT as Logic	235	0	0	230400	0.10
LUT as Memory	0	0	0	101760	0.00
CLB Registers	83	0	0	460800	0.02
Register as Flip Flop	83	0	0	460800	0.02
Register as Latch	0	0	0	460800	0.00
CARRY8	6	0	0	28800	0.02
F7 Muxes	0	0	0	115200	0.00
F8 Muxes	0	0	0	57600	0.00
F9 Muxes	0	0	0	28800	0.00
Site Type	Used	Fixed	Prohibited	Available	Util%
Block RAM Tile	0	0	0	312	0.00
RAMB36/FIFO*	0	0	0	312	0.00
RAMB18	0	0	0	624	0.00
URAM	0	0	0	96	0.00

BRAM usage

Since this design's RAMs are not the inner design's RAM, the synthesis report might not generate the BRAM in used.

Ref Name	Used	Functional Category
OBUF	169	I/O
INBUF	159	I/O
IBUFCTRL	159	Others
LUT2	83	CLB
FDCE	78	Register
LUT3	68	CLB
LUT4	64	CLB
LUT6	37	CLB
LUT5	29	CLB
CARRY8	6	CLB
FDPE	5	Register
DSP48E2	3	Arithmetic
LUT1	1	CLB
BUFGCE	1	Clock


Nearly all the logics being synthesized are generated into LUT.


Timing report

From Clock: axis_clk
To Clock: axis_clk

Setup :	0 Failing Endpoints, Worst Slack	1.306ns, Total Violation	0.000ns
Hold :	NA Failing Endpoints, Worst Slack	NA , Total Violation	NA
PW :	0 Failing Endpoints, Worst Slack	5.725ns, Total Violation	0.000ns

Waveform

 

 

ap_done at 79235 ns

The total computing latency: $(79235 - 1095) / 10\text{ns} = 7814$ cycles